

**NETWORK ANALYSIS**

(Common to ECE, EIE, E.Con.E &amp; ECC)

Time: 3 hours


Max. Marks: 80

Answer any FIVE questions


All questions carry equal marks

\*\*\*\*\*

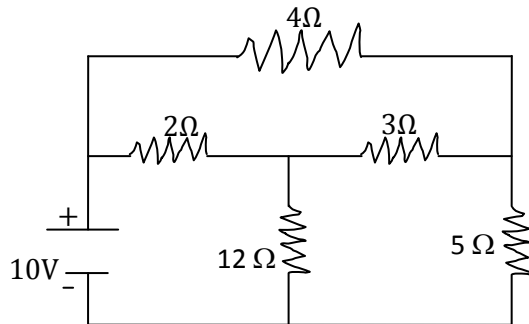- 1 (a) Three resistances  $R_{ab}$ ,  $R_{bc}$  and  $R_{ca}$  are connected in delta connection, derive the expressions for equivalent star connection.
- (b) Find the current supplied by 10 V battery by using star-delta transformation for the following network.




- 2 (a) Derive the expression for RMS value of alternating current wave  $i = I_m \sin \omega t$ .
- (b) A coil takes a current of 1 A at 0.6 lagging power factor from a 220 V, 60 Hz single phase source. If the coil is modeled by a series RL circuit find (i) The complex power in the coil and (ii) The values of R and L.
- 3 (a) Derive the relation between phase and line values in three phase star connected balanced system.
- (b) Given a series RLC circuit with  $R = 100 \text{ ohms}$ ,  $L = 0.5 \text{ H}$  and  $C = 40 \text{ } \mu\text{F}$ , calculate the resonant, lower and upper half – power frequencies.
- 4 For the below network draw the graph and write down the procedure to obtain cut set matrix.

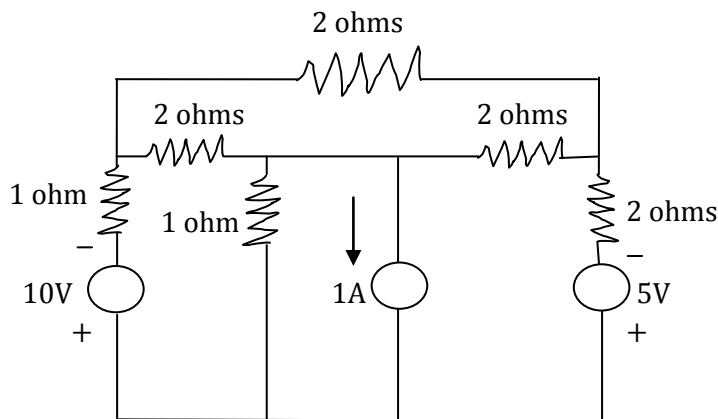

Contd. in page 2

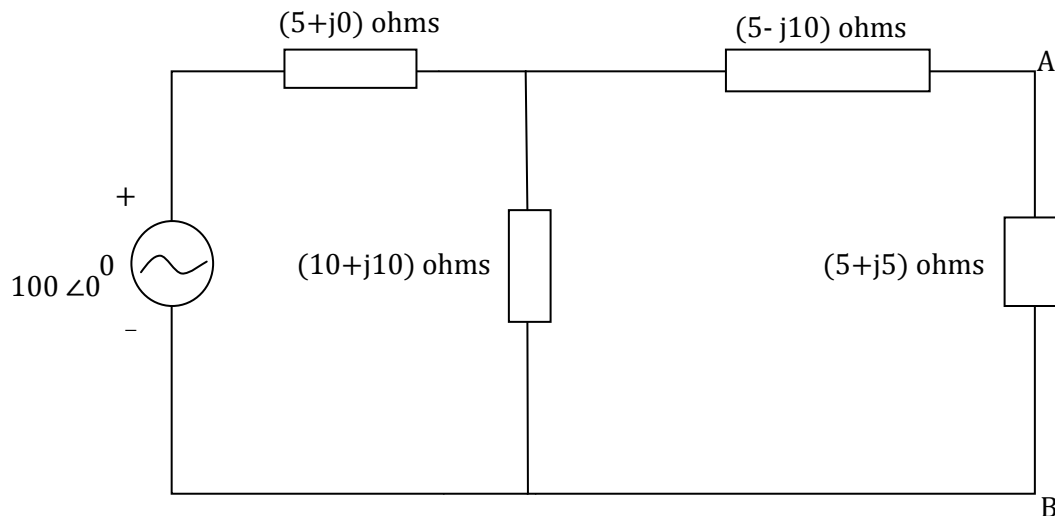- 5 (a) State and explain Millman's theorem for AC network by taking any one example.  
 (b) By using Norton's theorem find the current flowing through  $(5+j5)$  ohms impedance



- 6 (a) Derive the relation between Z and Y parameters in a two port network.  
 (b) Define and explain ABCD-parameters of a two port network.
- 7 (a) Derive the expression for  $i(t)$ , when series RLC circuit excited by DC voltage 'V' when the switch is closed at  $t = 0$ .  
 (b) In a series RLC circuit  $R = 5$  ohms,  $L = 1$  H,  $C = 1$  F. A DC voltage of 20 V is applied at  $t = 0$ . Obtain  $i(t)$ .
- 8 (a) Write short notes on m-derived high pass filter.  
 (b) Design m-derived high pass filter, given nominal impedance = 600 ohms,  $m = 0.45$  and cut off frequency = 10 KHz.

\*\*\*\*\*