

**NETWORK ANALYSIS**

(Common to ECE, EIE, E.Con.E &amp; ECC)


Time: 3 hours

Max. Marks: 80


Answer any FIVE questions  
All questions carry equal marks

\*\*\*\*\*

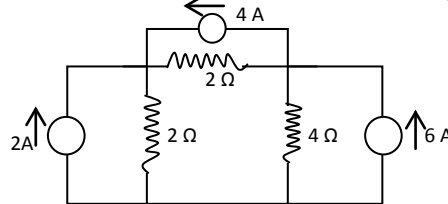
- 1 (a) State and explain the volt-ampere relationships for R, L, C parameters.  
(b) Using nodal analysis, find the current I in the circuit shown in figure given below.



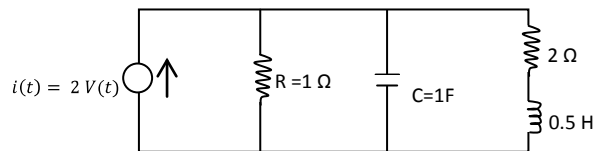
- (c) A  $5\mu\text{F}$  capacitor has charge  $q(t) = 100[1 + e^{-5 \times 10^4 t}]$  micro Coulombs. Determine the corresponding  $V(t)$  and  $i(t)$ .
- 2 (a) Define RMS value, average and form factor for a periodic quantity. Find the RMS values of:  
(i)  $V(t) = 25 \cos \omega t + 15 \sin \omega t$  and  
(ii)  $I(t) = 100 \sin \omega t - 10 \cos 2\omega t$   
(b) Determine  $V_c(t)$  and  $i_L(t)$  in the circuit shown below. Assume zero initial conditions. Use Laplace transforms method.



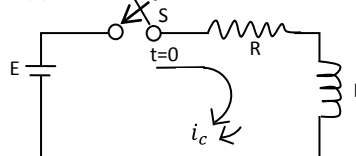- 3 (a) The voltage applied to a circuit and the current drawn are  $V = (200 - j100)$  V and  $I = (60 + j40)$  A respectively. Determine the circuit parameters and power dissipated.  
(b) Derive the expression for  $i(t)$  when the switch S is suddenly closed at  $t = 0$  in the circuit shown below. Sketch the variation of  $i(t)$  with respect to time.



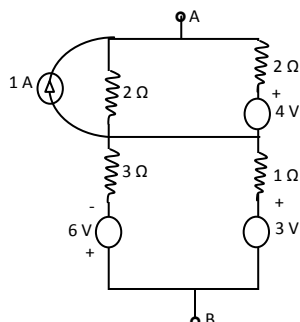
- (c) A series RLC circuit has  $R = 10 \Omega$ ,  $L = 0.01$  H and  $C = 100 \mu\text{F}$ . Find  
(i) Resonance frequency.  
(ii) Q factor.  
(iii) Band width of the circuit.
- 4 (a) Define and explain the following with an example.  
(i) Oriented graph. (ii) Tree of a graph.  
(iii) Cutset & a basic cutset. (iv) Tieset & a basic tieset.  
(b) Using source transformation, reduce the network between A & B shown below into an equivalent voltage source.



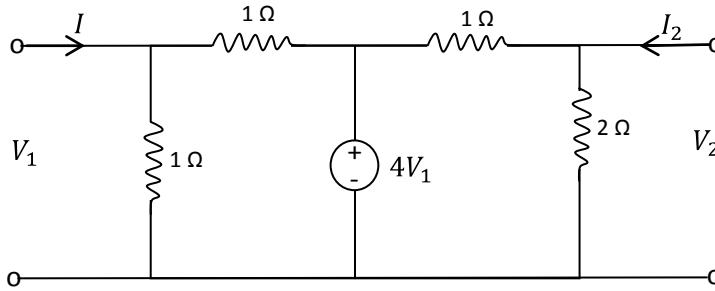- (c) What is duality? Explain the procedure for drawing the dual of given network with an example.


Contd. in Page no 2

- 5 (a) Why Z-parameters are known as open circuit parameters?  
 (b) What is meant by port? Explain two port networks.  
 (c) Obtain 'y' parameters for the network shown in figure below.




- 6 (a) A coil of 500 turns is wound uniformly over a wooden ring having a mean circumference of 50 cms and a cross sectional area of  $500 \text{ mm}^2$ . If the current through the coil is 3 A, calculate:  
 (i) The magnetic field strength.  
 (ii) The flux density and  
 (iii) The total flux.  
 (b) Define magneto motive force, magnetic flux density, magnetizing force and reluctance in a magnetic circuit.  
 (c) Derive the expression for coefficient coupling between pair of magnetically coupled coils.

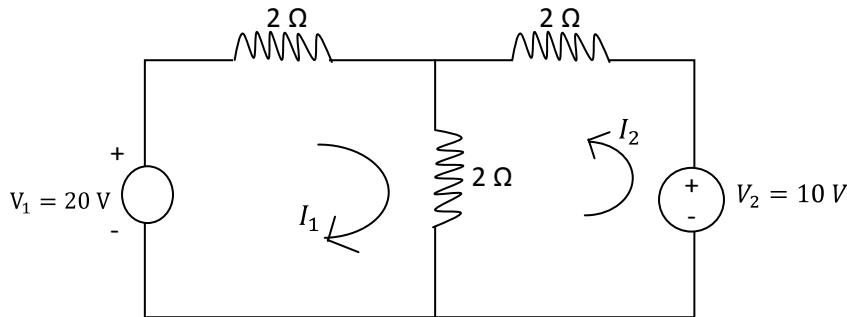- 7 (a) Define & verify Tellegen's theorem in the network shown below.



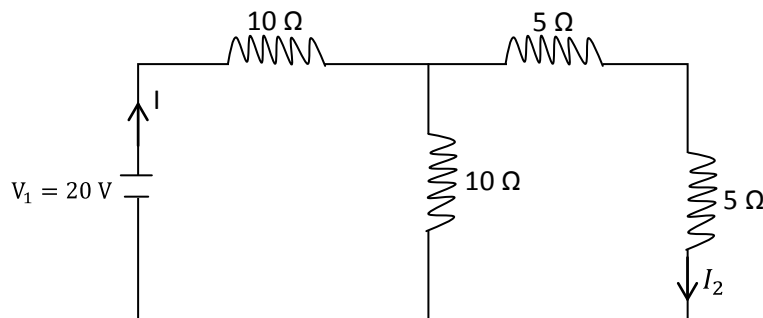- (b) Define & verify the reciprocity theorem for the network shown below.



- 8 (a) Discuss about m derived low pass T-section and  $\pi$  section in detail.  
 (b) Discuss about the variation of attenuation, phase shift and characteristic impedance of m derived high pass filter.

\*\*\*\*\*