

G. PULLAIAH COLLEGE OF ENGINEERING AND TECHNOLOGY

Accredited by NAAC with 'A' Grade of UGC, Approved by AICTE, New Delhi

Permanently Affiliated to JNTUA, Ananthapuramu

(Recognized by UGC under 2(f) and 12(B) & ISO 9001:2008 Certified Institution)

Nandikotkur Road, Venkayapalli, Kurnool – 518452

Department of Electronics and Communication Engineering

***Bridge Course
On
Computer Organization***

Number Systems:

- 1) Binary Number system: Digits used are 0,1. Base of this system is 2.
- 2) Decimal Number System: Digits used are 0,1,2,3,4,5,6,7,8,9. Base of the system is 10.
- 3) Octal Number System: Digits used are 0,1,2,3,4,5,6,7. Base of the system is 8.
- 4) Hexa Decimal Number System: Digits used are 0,1,2,3,4,5,6,7,8,9,A,B,C,D,E,F. Base of the system is 16.

Hex	Decimal	Octal	Binary
0	0	0	0
1	1	1	1
2	2	2	10
3	3	3	11
4	4	4	100
5	5	5	101
6	6	6	110
7	7	7	111
8	8	10	1000
9	9	11	1001
A	10	12	1010
B	11	13	1011
C	12	14	1100
D	13	15	1101
E	14	16	1110
F	15	17	1111
10	16	20	10000

Number Conversions:

1) Octal to Decimal

Eg: Convert $(125)_8 = ()_{10}$

$$1 \times 8^2 + 2 \times 8^1 + 5 \times 8^0 = 64 + 16 + 5 = 85_{10}$$

2) Hex to Decimal

Eg: Convert $(1A3)_{16} = ()_{10}$

$$1 \times 16^2 + A \times 16^1 + 3 \times 16^0 = 256 + 160 + 3 = 419_{10}$$

3) Binary to Decimal

Eg: Convert $(10111)_2 = ()_{10}$

$$1 \times 2^4 + 0 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 1 \times 2^0 = 16 + 0 + 4 + 2 + 1 = 23$$

4) Decimal to Binary

Eg: Convert $(395)_{10} = ()_2$

$$\begin{array}{r} 2)395 \\ \hline 2)197-1 \\ \hline 2)98-1 \\ \hline 2)49-0 \\ \hline 2)24-1 \\ \hline 2)12-0 \\ \hline 2)6-0 \\ \hline 2)3-0 \\ \hline 2)1-1 \\ \hline \end{array}$$

$$(110001011)_2$$

5) Decimal to Octal

Eg: Convert $(395)_{10} = ()_8$

$$\begin{array}{r} 8)395 \\ \hline 8)49-3 \\ \hline 8)6-1 \\ \hline \end{array} = (613)_8$$

6) Decimal to Hex

Eg: Convert $(1029)_{10} = ()_{16}$

$$\begin{array}{r} 16)1029 \\ \hline 16)64-5 \\ \hline 16)4-0 \\ \hline \end{array} = (405)_{16}$$

7) Binary to Octal

Eg: Convert $(10110111101)_2 = ()_8$

$$= 10 \ 110 \ 111 \ 101 = (2675)_8$$

8) Binary to Hex

Eg: Convert $(1011011110110)_2 = ()_{16}$

$$= 1 \ 0110 \ 1111 \ 0110 = (16F6)_{16}$$

1's Complement:

Subtract the given number from all 1s or flip 1 to 0 and 0 to 1.

Eg: Find 1's complement of 11001_2

$$\begin{array}{r} 11111 \\ 11001 \\ \hline 00110 \end{array}$$

1's complement is used to store the negative numbers. Disadvantage of this system is +0 and -0 are having different values.

2's Complement:

Find 1's complement of the given number and add 1 to the answer.

Eg: Find 2's complement of 11001_2

1's complement of 11001 is $00110 + 1 = 00111$.

In this system +0 and -0 are having same representation. Hence 2's complement is used to store the -ve numbers in memory.


Floating Point Numbers

Logic Gates:

AND GATE


A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

$$Y = ABC$$

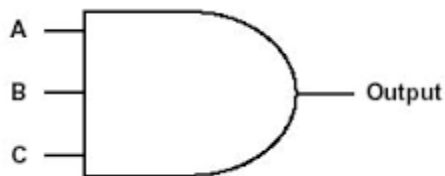


OR GATE

A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

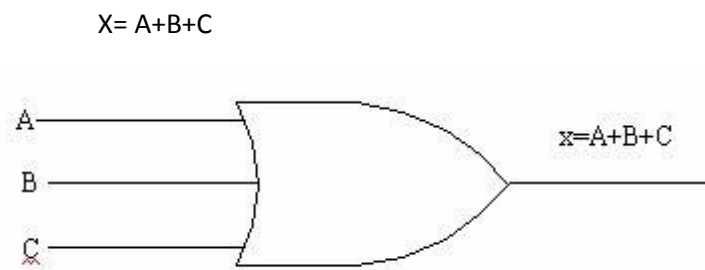


NOT GATE

A	Q
0	1
1	0

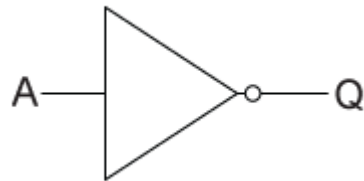

NAND GATE

A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1

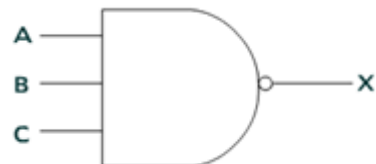


1	1	1	0
---	---	---	---

$$X = (ABC)'$$

NOR GATE


A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$$F = (A+B+C)'$$

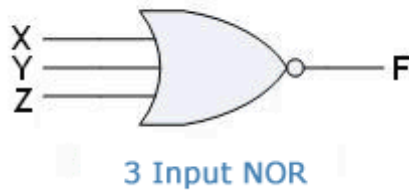

XOR GATE



A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

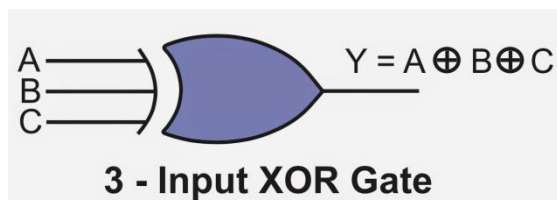

Combinational Circuits:

1. Decoder : It will have n inputs and $2n$ outputs. Out of all outputs only one will be selected.



2 to 4 Decoder

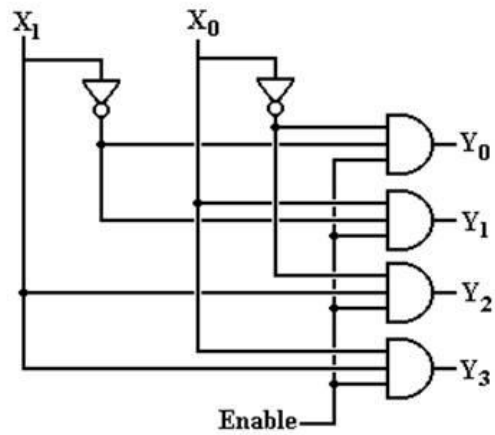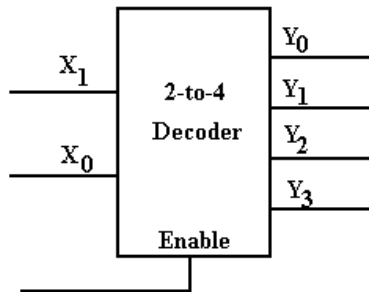

Truth Table



X_1	X_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

3 to 8 Decoder

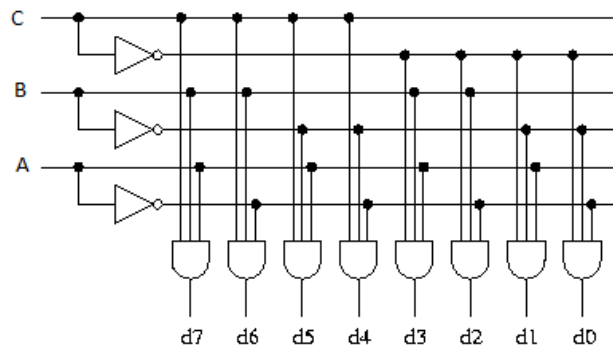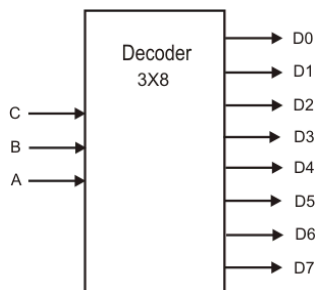


C	B	A	D7	D6	D5	D4	D3	D2	D1	D0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

Multiplexer
2:1 MUX

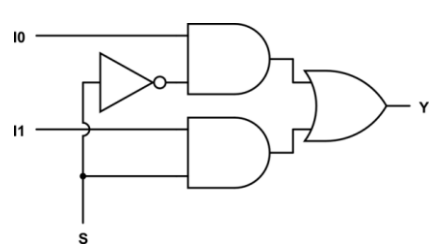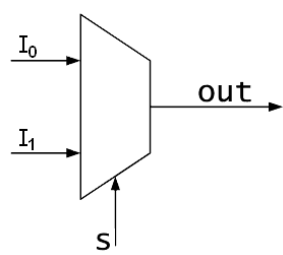

S	Out
0	I ₀
1	I ₁

4:1 Mux

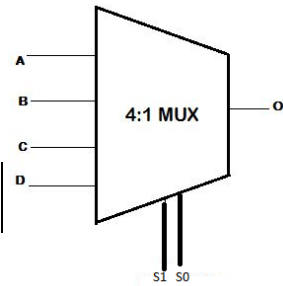

Truth


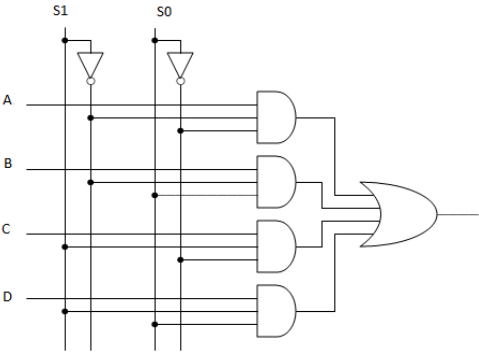
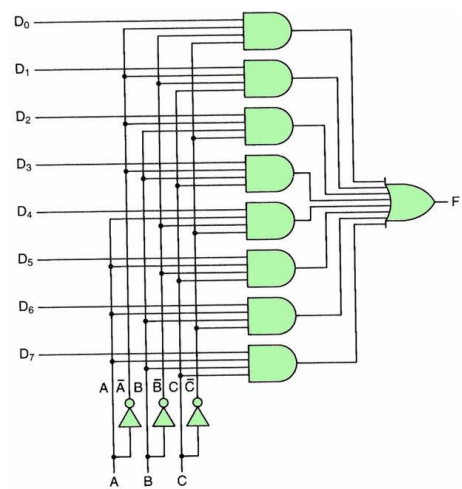


Table:

0	0	A
0	1	B
1	0	C
1	1	D

8:1 Mux

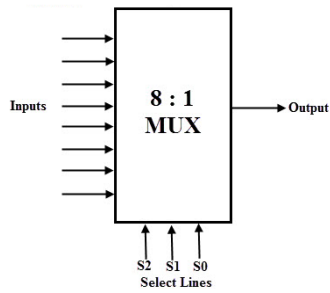



Truth Table

S2	S1	S0	O
0	0	0	I0
0	0	1	I1
0	1	0	I2
0	1	1	I3
1	0	0	I4
1	0	1	I5
1	1	0	I6
1	1	1	I7



Half Adder

Inputs		Outputs	
A	B	S	C
0	0	0	0
1	0	1	0
0	1	1	0
1	1	0	1

Truth table

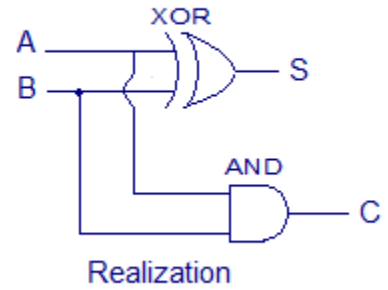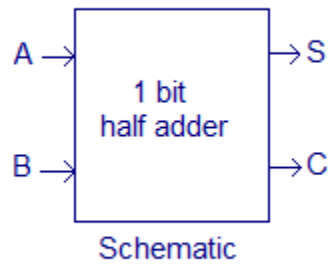

Full Adder

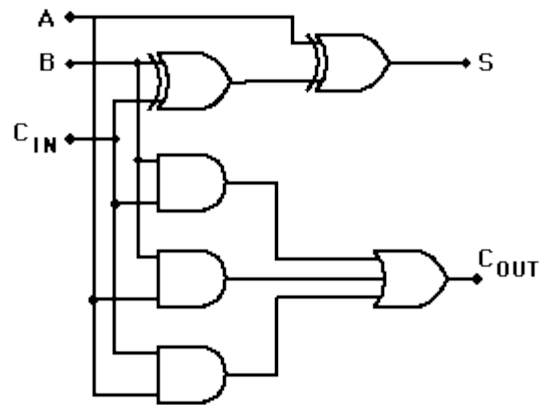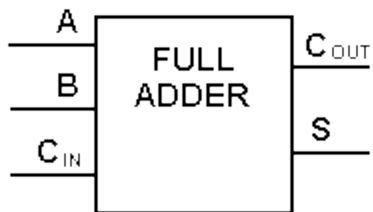

Input			Output	
A	B	C _{in}	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

4bit Adder

