

Part A - Compulsory question

	Question	Marks	Unit	CO	Cognitive level
1. (A)	Draw the circuit of RL and RC High pass filter	2	I	C218.1	Remember
(B)	Write the expression for Time Shifting property in relation to Fourier series	2	I	C218.1	Apply
(C)	Write the limitations of pspice	2	I	C218.1	Remember
(D)	Write the condition to be satisfied by a constant k filter	2	II	C218.1	Remember
(E)	Express dirichlet 's condition	2	II	C218.1	Remember


Part B – Answer one from 2 or 3 and one from 4 or 5

2.	A 50 Hz, 400 V (peak value) sinusoidal voltage is applied at $t = 0$ to a series RL circuit having resistance 5 ohms and inductance 0.2 mH. Obtain an expression for current at any instant 't', calculate the value of transient current 0.001 sec after switching ON.	10	I	C218.1	Analyze
3.	Discuss about the variation of attenuation, phase shift and characteristic impedance of m derived high pass filter.	10	I	C218.1	Analyze
4.	Derive the Fourier transform of a single rectangular pulse of width τ and height A.	10	II	C218.5	Analyze
5.	Obtain the expression for $i(t)$ for a series RC circuit when excited by a pulse source of Width 'a' using Laplace transform method	10	II	C218.5	Analyze

Part A - Compulsory question

	Question	Marks	Unit	CO	Cognitive level
1. (A)	What do you mean by the term filter? List the types of filters	2	II	C218.1	Remember
(B)	Draw the circuit of RL and RC Low pass filter	2	I	C218.1	Apply
(C)	Write the limitations of pspice	2	II	C218.1	Remember
(D)	Express Z_{OT} in terms of Z_{SC} and Z_{OC}	2	I	C218.1	Remember
(E)	Explain in brief variation of characteristic impedance in pass band and stop band.	2	II	C218.1	Apply

Part B – Answer one from 2 or 3 and one from 4 or 5

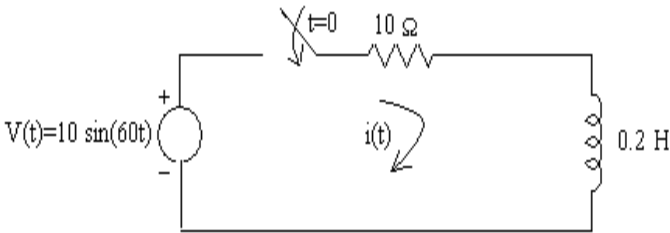2.	<p>A series RL circuit is shown in figure below. If the switch 'K' in the circuit is closed at $t=0$, Find an expression for $i(t)$.</p> 	10	I	C218.1	Analyze
3.	Design a m-derived low filter with a design impedance of 300Ω and the cut off frequency at 2 KHz and infinite attenuation at 2345Hz.	10	I	C218.1	Analyze
4.	Derive the Fourier series of a half wave rectifier by drawing a neat wave form.	10	II	C218.5	Analyze
5.	Derive the expression of characteristic impedance for both T & π networks	10	II	C218.5	Analyze

Part A - Compulsory question

	Question	Marks	Unit	CO	Cognitive level
1. (A)	Draw the frequency response of high pass filters.	2	I	C218.1	Remember
(B)	Write short notes on dirichlet's conditions for Fourier series.	2	I	C218.1	Apply
(C)	Define the term Decibel	2	I	C218.1	Remember
(D)	Define time constant	2	II	C218.1	Remember
(E)	Explain about phase spectra	2	II	C218.1	Remember



Part B – Answer one from 2 or 3 and one from 4 or 5

2.	Obtain the expression for $i(t)$ for a series RL circuit when excited by a source of $V(t)=V_m \sin(\omega t+\theta)$ using Laplace transform	10	I	C218.1	Analyze
3.	A) Categorize filters and explain in brief about m-derived High pass filter B) Design a m-derived low pass filter with a design impedance of 500Ω and the cut off frequency at 5 KHz and infinite attenuation at 5365Hz.	5 5	I	C218.1	Analyze
4.	Derive the Fourier series of a square wave drawing a neat wave form.	10	II	C218.5	Analyze
5.	A series RL circuit with $R= 50 \Omega$ and $L=0.2 \text{ H}$ has a sinusoidal voltage source $V=150 \sin(500 t)$ volts applied at $t=0$ Find the expression for total current.	10	II	C218.5	Analyze

Part A - Compulsory question

	Question	Marks	Unit	CO	Cognitive level
1. (A)	What are the disadvantages of constant – k filters	2	I	C218.1	Remember
(B)	Mention the frequency limits of low and high pass filters	2	I	C218.1	Apply
(C)	Write the expressions for Fourier coefficients?	2	I	C218.1	Remember
(D)	Define the term neper	2	II	C218.1	Remember
(E)	Define time constant	2	II	C218.1	Remember

Part B – Answer one from 2 or 3 and one from 4 or 5

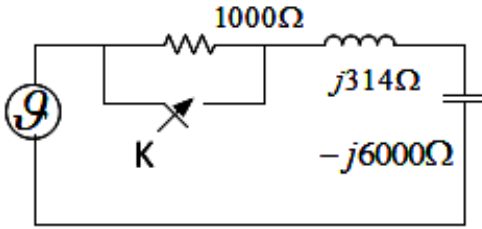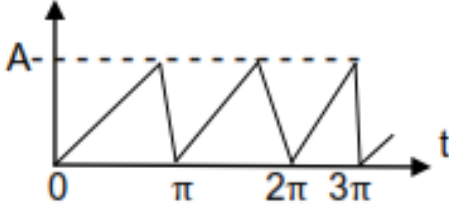2.	<p>With the switch open steady state is reached with $V = 100 \sin 314 t$ volts. The switch is closed at $t=0$. The circuit is allowed to come to steady state again. Determine steady state current and complete solution of transient current.</p> 	10	I	C218.1	Analyze
3.	<p>Determine the Fourier series of the given wave form.</p> 	10	I	C218.1	Analyze
4.	Explain about PSPICE Programming in detail.	10	II	C218.5	Understand And remember
5.	Design a Composite low pass filter with a design impedance of 600Ω and the cut off frequency of 2 KHz and infinite attenuation at 2100 Hz	10	II	C218.5	Analyze