

Sub: RF IC (13A04804)

Time: 1½ Hrs.

Date: 16-02-2018

Max Marks: 30M

Question 1 is compulsory. Answer one from 2 or 3 and one from 4 or 5.

S.No.	Questions	Marks	Unit	CO	Cognitive Level
1	a) What are the conditions for resonance in parallel RLC networks ?	2	1	C410.1	Remember
	b) Draw the circuits for tuned amplifier.	2	2	C410.1	Apply
	c) What is the image resistance?	2	1	C410.1	Remember
	d) Define the reflection coefficient?	2	1	C410.2	Remember
	e) Difference between lumped and distributed parameters?	2	2	C410.2	Understand
2	Explain in detail the basic architecture of Radio Frequency system?	10	1	C410.1	Understand
3	Explain in detail pi and T- matching of a network?	10	1	C410.1	Understand
4	Explain the open circuit time constant to estimate the band width of a given circuit With examples.	10	2	C410.2	Understand
5	Draw & Analyze the circuit diagram for CS- amplifier for a single tuned load & the Cascaded Amplifier.	10	2	C410.2	Understand & Apply

Sub: RF IC (13A04804)

Time: 1½ Hrs.

Date: 16-02-2018

Max Marks: 30M

Question 1 is compulsory. Answer one from 2 or 3 and one from 4 or 5.

S.No.	Questions	Marks	Unit	CO	Cognitive Level
1	a) What are the conditions for resonance in parallel RLC networks ?	2	1	C410.1	Remember
	b) Draw the circuits for tuned amplifier.	2	2	C410.1	Apply
	c) What is the image resistance?	2	1	C410.1	Remember
	d) Define the reflection coefficient?	2	1,2	C410.2	Remember
	e) Difference between lumped and distributed parameters?	2	2	C410.2	Understand
2	Explain in detail the basic architecture of Radio Frequency system?	10	1	C410.1	Understand
3	Explain in detail pi and T- matching of a network?	10	1	C410.1	Understand
4	Explain the open circuit time constant to estimate the band width of a given circuit With examples.	10	2	C410.2	Understand
5	Draw & Analyze the circuit diagram for CS- amplifier for a single tuned load & the Cascaded Amplifier.	10	2	C410.2	Understand & apply

Sub: RF IC (13A04804)

Time: 1½ Hrs.

Date: 16-02-2018

Max Marks: 30M

Question 1 is compulsory. Answer one from 2 or 3 and one from 4 or 5.

S.No.	Questions	Marks	Unit	CO	Cognitive Level
1	a) State the Maximum power transfer theorem & its conditions?	2	1	C410.1	Remember
	b) what is the relation between the gain and bandwidth factor?	2	1	C410.1	Remember
	c) Draw the circuits for tuned amplifier.	2	2	C410.2	Apply
	d) What are the conditions for resonance in parallel RLC networks ?	2	1	C410.2	Remember
	e) How do you know the accuracy of OCTC & SCTC methods?	2	2	C410.2	Understand
2	Design and convert Series to parallel RL & RC network Transformations?	10	1	C410.1	Understand
3	Explain in detail the basic architecture of Radio Frequency system?	10	1	C410.1	Understand
4	Prove that a long channel MOS device transconductance depends only on the square root of bias current?	10	2	C410.2	Apply
5	Explain the Short circuit time constant to estimate the band width of a given circuit. With examples ?	10	2	C410.2	Understand

Sub: RF IC (13A04804)

Time: 1½ Hrs.

Date: 16-02-2018

Max Marks: 30M

Question 1 is compulsory. Answer one from 2 or 3 and one from 4 or 5.

S.No.	Questions	Marks	Unit	CO	Cognitive Level
1	a) State the Maximum power transfer theorem & its conditions?	2	1	C410.1	Remember
	b) what is the relation between the gain and bandwidth factor?	2	1	C410.1	Remember
	c) Draw the circuits for tuned amplifier.	2	2	C410.2	Remember
	d) What are the conditions for resonance in parallel RLC networks ?	2	1	C410.2	Remember
	e) How do you know the accuracy of OCTC & SCTC methods?	2	2	C410.2	Understand
2	Design and convert Series to parallel RL & RC network Transformations?	10	1	C410.1	Understand
3	Explain in detail the basic architecture of Radio Frequency system?	10	1	C410.1	Understand
4	Prove that a long channel MOS device transconductance depends only on the square root of bias current?	10	2	C410.2	Understand
5	Explain the Short circuit time constant to estimate the band width of a given circuit. With examples ?	10	2	C410.2	Understand

Sub: RF IC (13A04804)
Time: 1½ Hrs.

Date: 16-02-2018
Max Marks: 30M

Question 1 is compulsory. Answer one from 2 or 3 and one from 4 or 5.

S.No.	Questions	Marks	Unit	CO	Cognitive Level
1	a) What is reflection coefficient in RF system?	2	1	C410.1	Analyze
	b) What are the conditions for resonance in parallel RLC networks ?	2	1	C410.1	Remember
	c) How do you know the accuracy of OCTC & SCTC methods?	2	2	C410.2	Understand
	d) State the relation between B.W & Rise time for Ist order systems?	2	2	C410.2	Understand
	e) What is LNA & PA?	2	1	C410.1	Remember
2	Explain in detail the basic architecture of Radio Frequency system?	10	1	C410.1	Understand
3	Explain in detail pi and T- matching of a network?	10	1	C410.1	Understand
4	Prove that a long channel MOS device transconductance depends only on the square root of bias current?	5	2	C410.2	Remember
5	Explain the Short circuit time constant to estimate the band width of a given circuit. With examples ?	10	2	C410.2	Understand

Sub: RF IC (13A04804)
Time: 1½ Hrs.

Date: 16-02-2018
Max Marks: 30M

Question 1 is compulsory. Answer one from 2 or 3 and one from 4 or 5.

S.No.	Questions	Marks	Unit	CO	Cognitive Level
1	a) What is reflection coefficient in RF system?	2	1	C410.1	Analyze
	b) What are the conditions for resonance in parallel RLC networks ?	2	1	C410.1	Remember
	c) How do you know the accuracy of OCTC & SCTC methods?	2	2	C410.2	Understand
	d) State the relation between B.W & Rise time for Ist order systems?	2	2	C410.2	Understand
	e) What is LNA & PA?	2	1	C410.1	Remember
2	Explain in detail the basic architecture of Radio Frequency system?	10	1	C410.1	Understand
3	Explain in detail pi and T- matching of a network?	10	1	C410.1	Understand
4	Prove that a long channel MOS device transconductance depends only on the square root of bias current?	5	2	C410.2	Analyze
5	Explain the Short circuit time constant to estimate the band width of a given circuit. With examples ?	10	2	C410.2	Understand

Sub: RF IC (13A04804)

Time: 1½ Hrs.

Date: 16-02-2018

Max Marks: 30M

Question 1 is compulsory. Answer one from 2 or 3 and one from 4 or 5.

S.No.	Questions	Marks	Unit	CO	Cognitive Level
1	a) What are the conditions for resonance in parallel RLC network?	2	1	C410.1	Remember
	b) What is the relation between the gain and bandwidth factor?	2	1	C410.1	Remember
	c) What is figure of merit for a Mos device?	2	2	C410.2	Analyze
	d)) How do you know the accuracy of OCTC & SCTC methods?	2	2	C410.2	Remember
	e) What is reflection coefficient in RF system?	2	2	C410.2	Remember
2	Design and convert Series to parallel RL & RC network Transformations?	10	1	C410.1	Understand
3	Explain in detail the basic architecture of Radio Frequency system?	10	1	C410.1	Understand
4	Prove that a long channel MOS device transconductance depends only on the square root of bias current?	10	2	C410.2	Analyze
5	Explain the circuit diagram for CS- amplifier for a single tuned load & the Cascaded Amplifier.	10	2	C410.2	Understand

Sub: RF IC (13A04804)

Time: 1½ Hrs.

Date: 16-02-2018

Max Marks: 30M

Question 1 is compulsory. Answer one from 2 or 3 and one from 4 or 5.

S.No.	Questions	Marks	Unit	CO	Cognitive Level
1	a) What are the conditions for resonance in parallel RLC network?	2	1	C410.1	Remember
	b) What is the relation between the gain and bandwidth factor?	2	1	C410.1	Remember
	c) What is figure of merit for a Mos device?	2	2	C410.2	Analyze
	d) How do you know the accuracy of OCTC & SCTC methods?	2	2	C410.2	Remember
	e) What is reflection coefficient in RF system?	2	2	C410.2	Remember
2	Design and convert Series to parallel RL & RC network Transformations?	10	1	C410.1	Understand
3	Explain in detail the basic architecture of Radio Frequency system?	10	1	C410.1	Understand
4	Prove that a long channel MOS device transconductance depends only on the square root of bias current?	10	2	C410.2	Analyze
5	Explain the circuit diagram for CS- amplifier for a single tuned load & the Cascaded Amplifier.	10	2	C410.2	Understand